







# Lecture 6

## - RC/RL First-Order Circuits



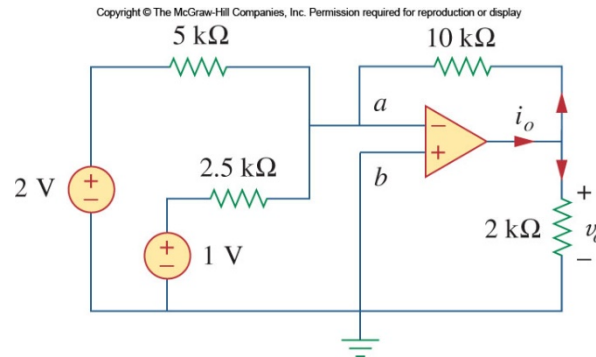
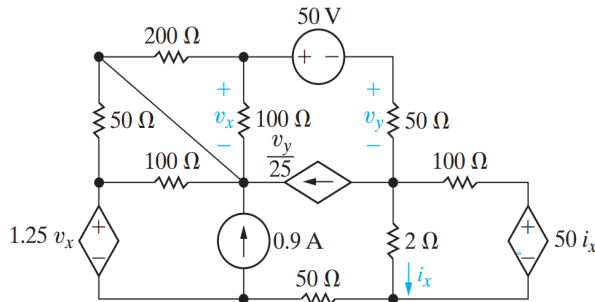
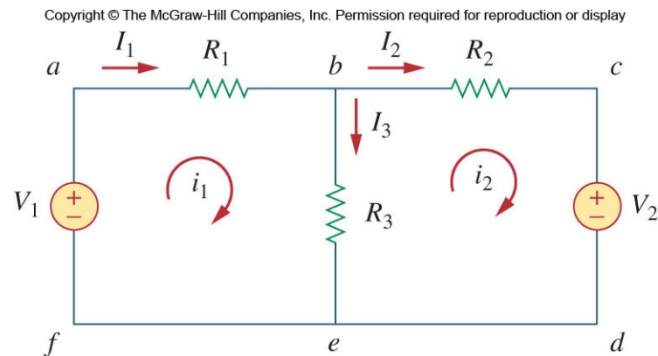
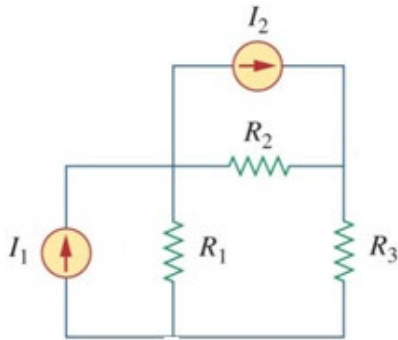
# Temporal Behavior of Circuit Responses

- Till now we discussed static analysis of a circuit
  - Responses at a given time depend only on inputs at that time.
  - Circuit responds to input changes infinitely fast.


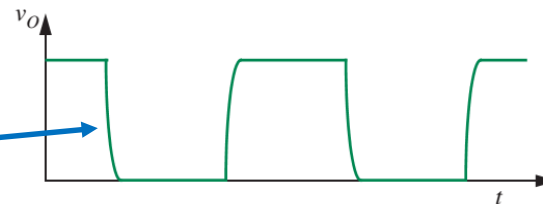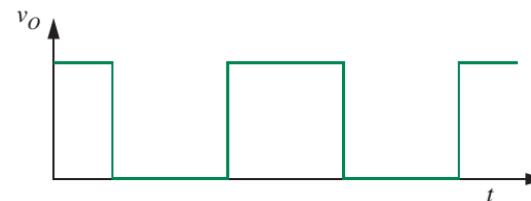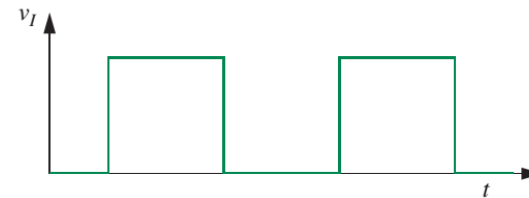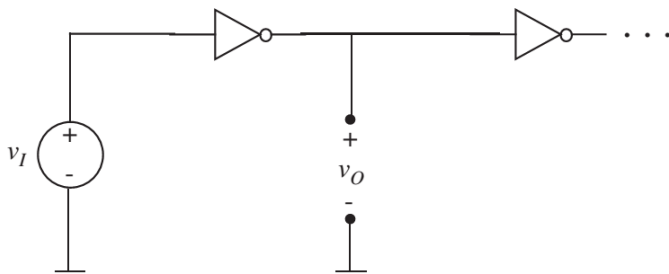
# Temporal Behavior of Circuit Responses

- From now on we start to discuss dynamic circuit
  - **Time-varying** sources and responses



We have to introduce capacitors and inductors to explain such temporal behavior.





# Outline

- Natural response of RC/RL circuits
- Step response of RC/RL circuits
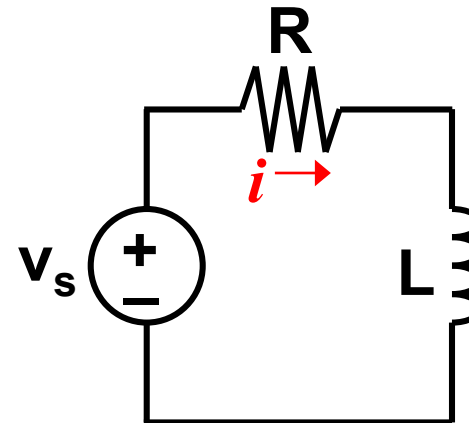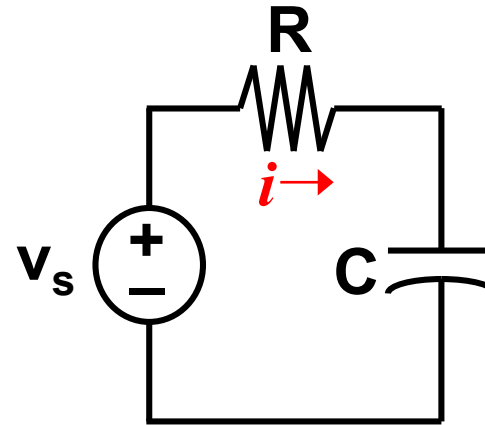
## RC and RL Circuits


- A circuit that contains only sources, resistors and a capacitor is called an **RC circuit**.
- A circuit that contains only sources, resistors and an inductor is called an **RL circuit**.






# RC and RL Circuits

## RC Circuit

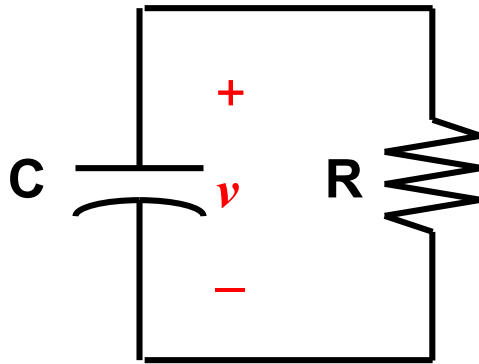

- Capacitor voltage cannot change instantaneously
- In steady state, a capacitor behaves like an open circuit

## RL Circuit

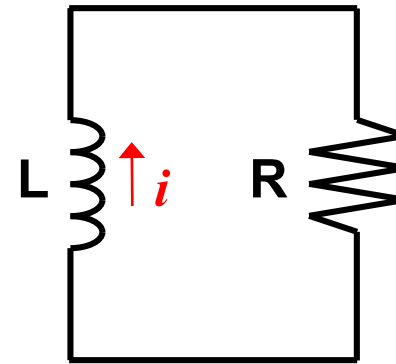


- Inductor current cannot change instantaneously
- In steady state, an inductor behaves like a short circuit.



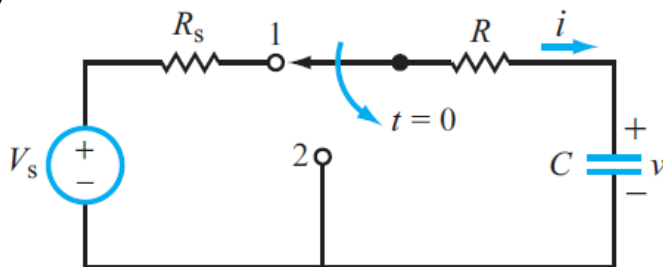
# Natural Response of a Charged Capacitor


Behavior (*i.e.*, current and voltage) when stored energy in the inductor or capacitor is released to the resistive part of the network (containing no independent sources).



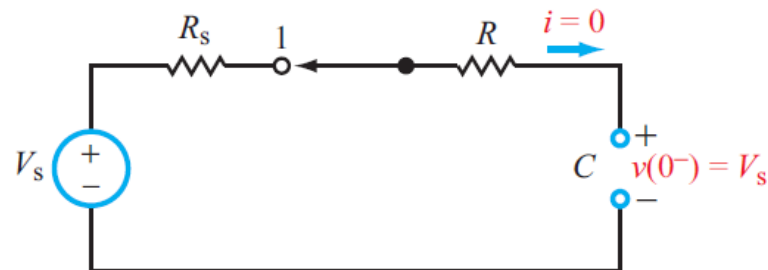(a)  $t = 0^-$  is the instant just before the switch is moved from terminal 1 to terminal 2;




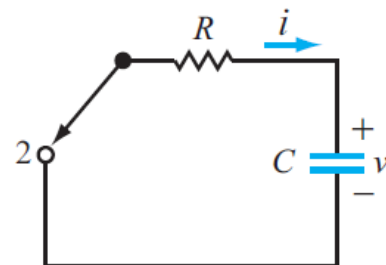(b)  $t = 0$  is the instant just after it was moved,  $t = 0$  is synonymous with  $t = 0^+$ .





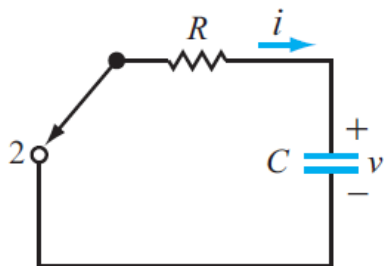
# Natural Response of a Charged Capacitor







# Natural Response of RC

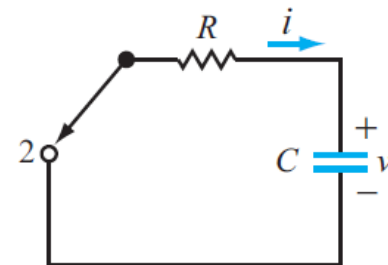


Time constant:  $\tau = RC$

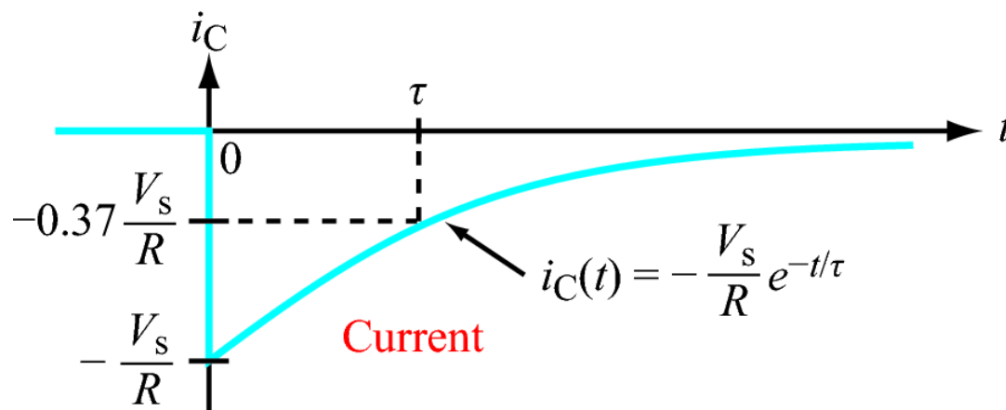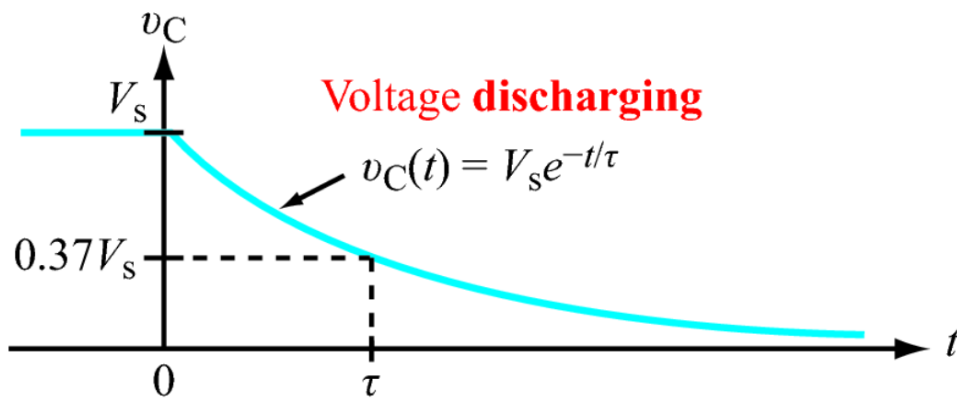
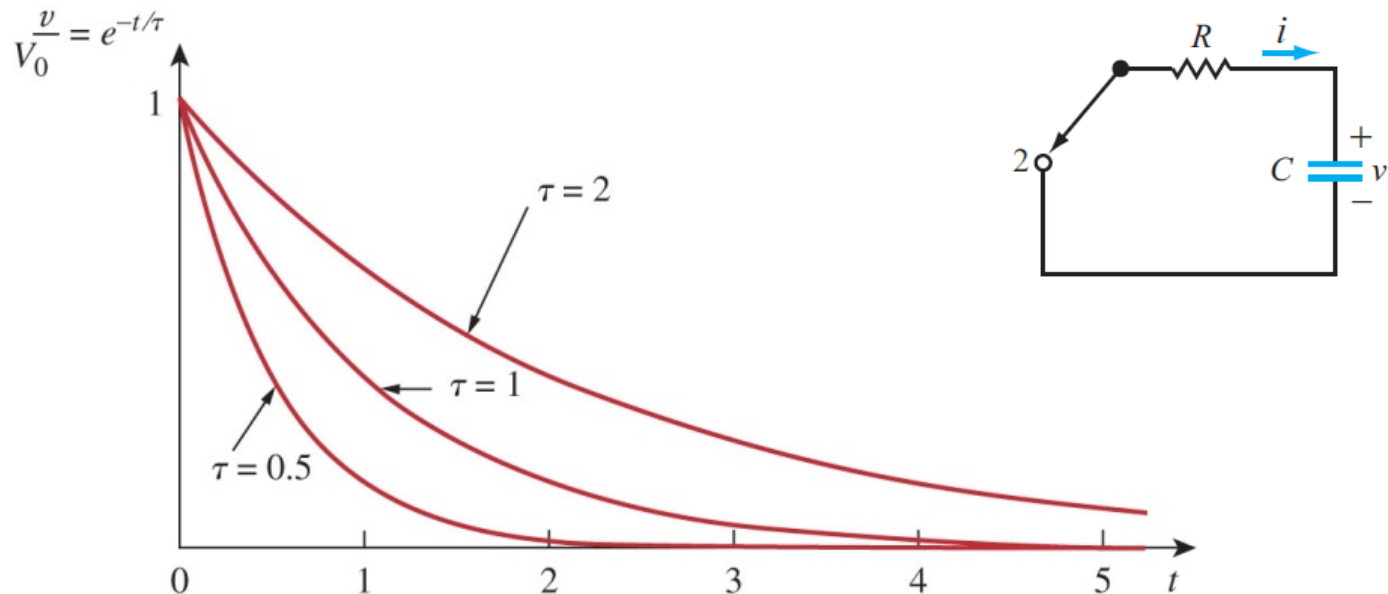
# Time Constant $\tau (= RC)$

- A circuit with a small time constant has a fast response and vice versa.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





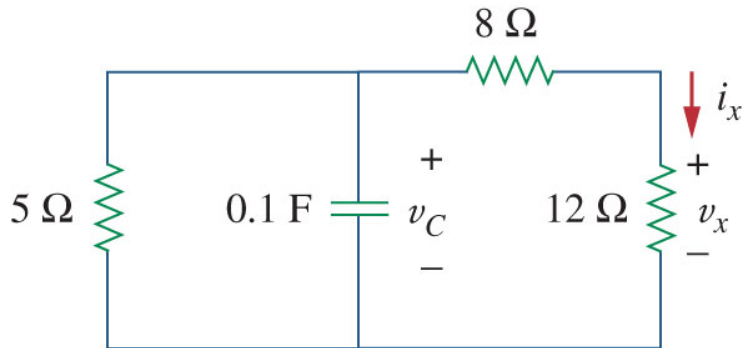
## Example




- In the circuit below, let  $v_C(0) = 15\text{V}$ . Find  $v_C$ ,  $v_x$ , and  $i_x$  for  $t > 0$ .

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display






# Natural Response of the RL Circuit

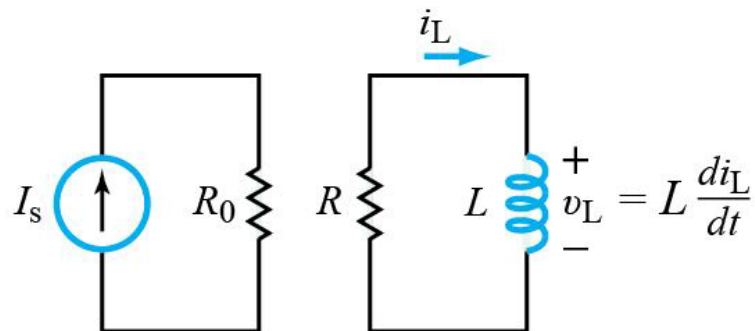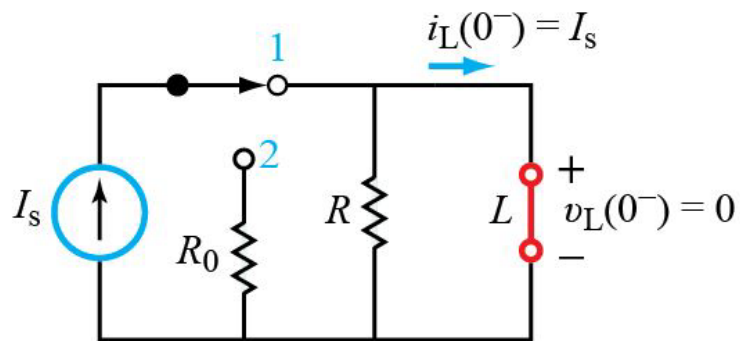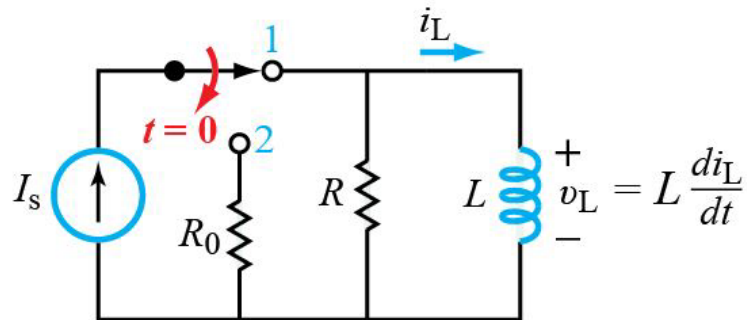




# Natural Response of the RL Circuit

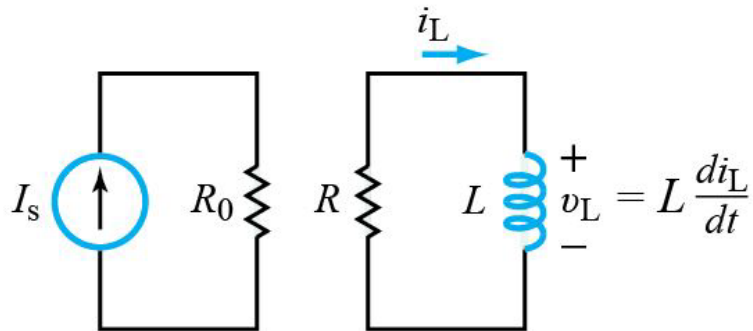



# Natural Response of the RL Circuit

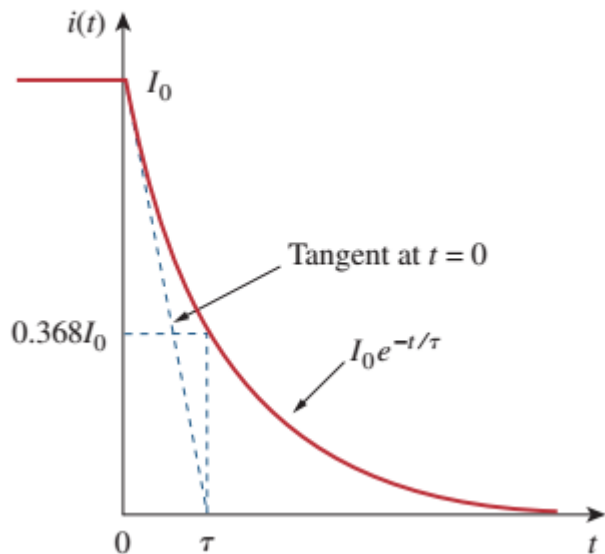




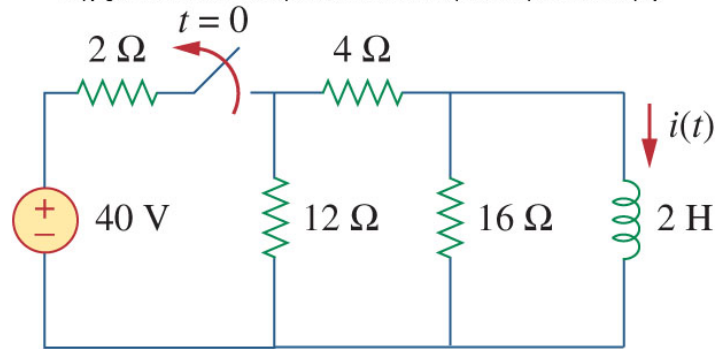
## Example

- The switch in the circuit below has been closed for a long time. At  $t = 0$ , the switch is opened. Calculate  $i(t)$  for  $t > 0$ .


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



When  $t < 0$

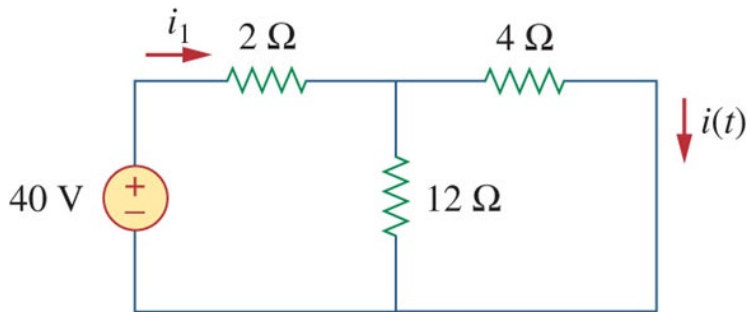


When  $t > 0$

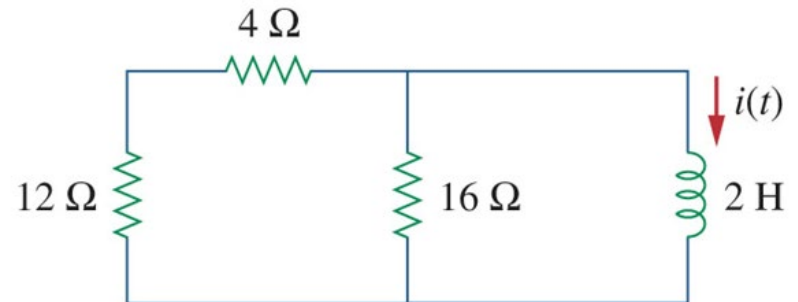



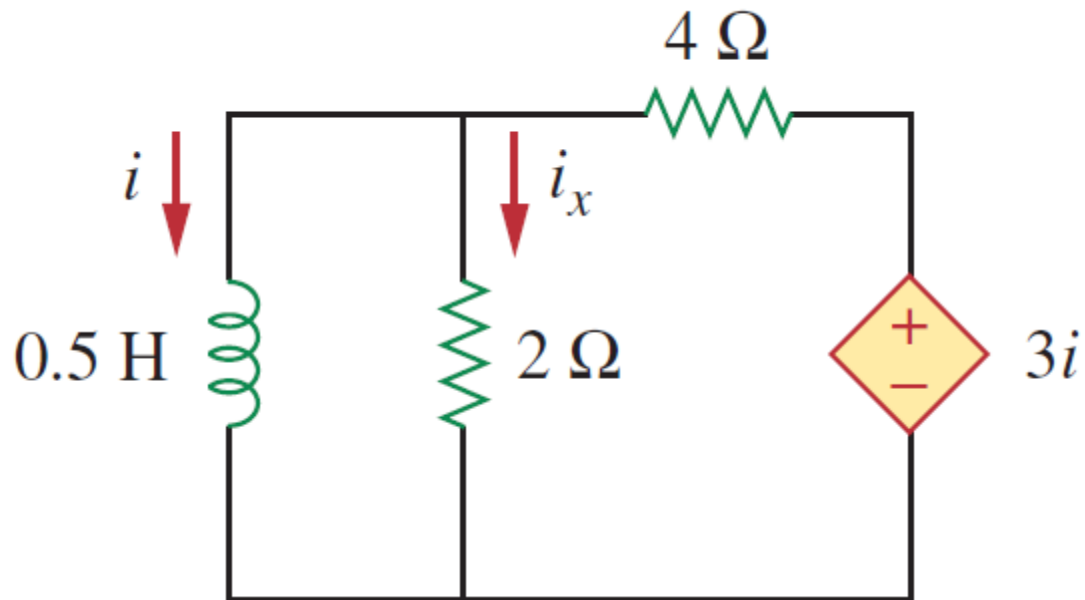
Assuming that  $i(0) = 10$  A, calculate  $i(t)$  and  $i_x(t)$





# Natural Response Summary

## RC Circuit

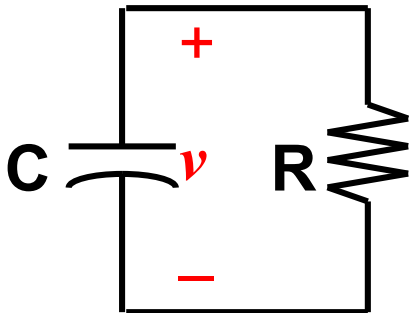


- **Capacitor voltage** cannot change instantaneously

$$v(0^-) = v(0^+)$$

$$v(t) = v(0)e^{-t/\tau}$$

- time constant  $\tau = RC$

## RL Circuit

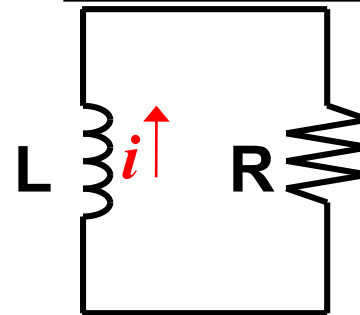

- **Inductor current** cannot change instantaneously



$$i(0^-) = i(0^+)$$

$$i(t) = i(0)e^{-t/\tau}$$

- time constant  $\tau = \frac{L}{R}$




**7.16** Determine the time constant for each of the circuits in Fig. 7.96.

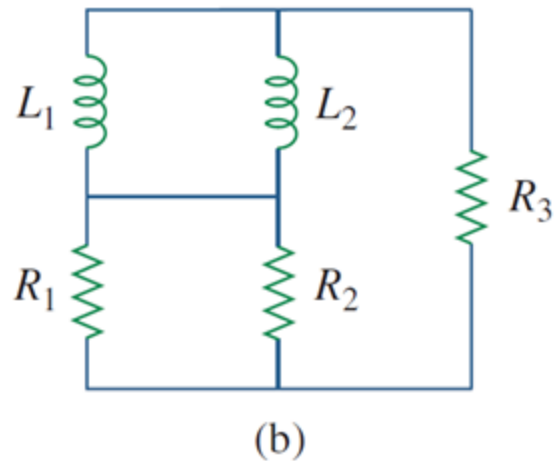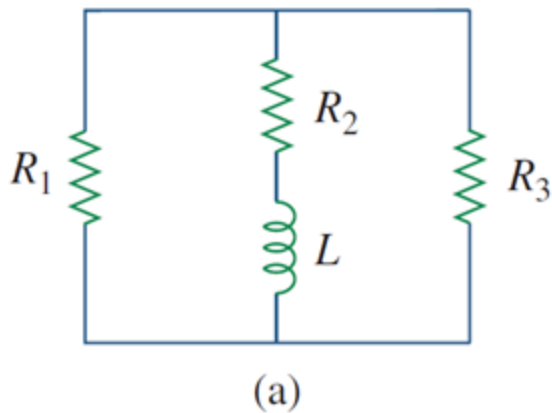

**Figure 7.96**  
For Prob. 7.16.



**7.19** In the circuit of Fig. 7.99, find  $i(t)$  for  $t > 0$  if  $i(0) = 6$  A.

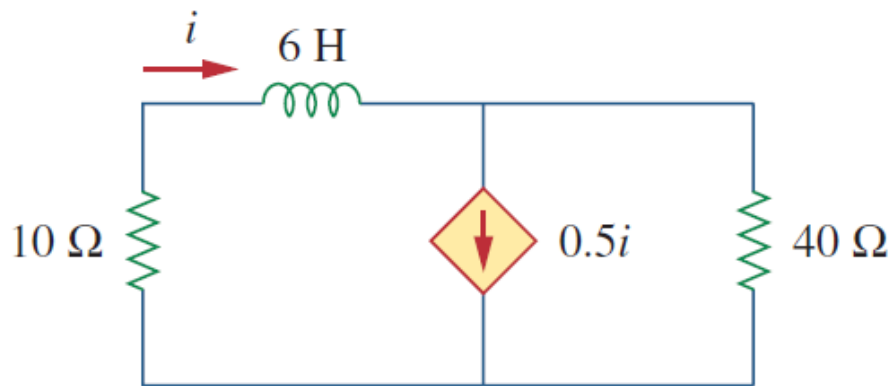

**Figure 7.99**  
For Prob. 7.19.




# Outline

- Natural response of RC/RL circuits
- Step response of RC/RL circuits
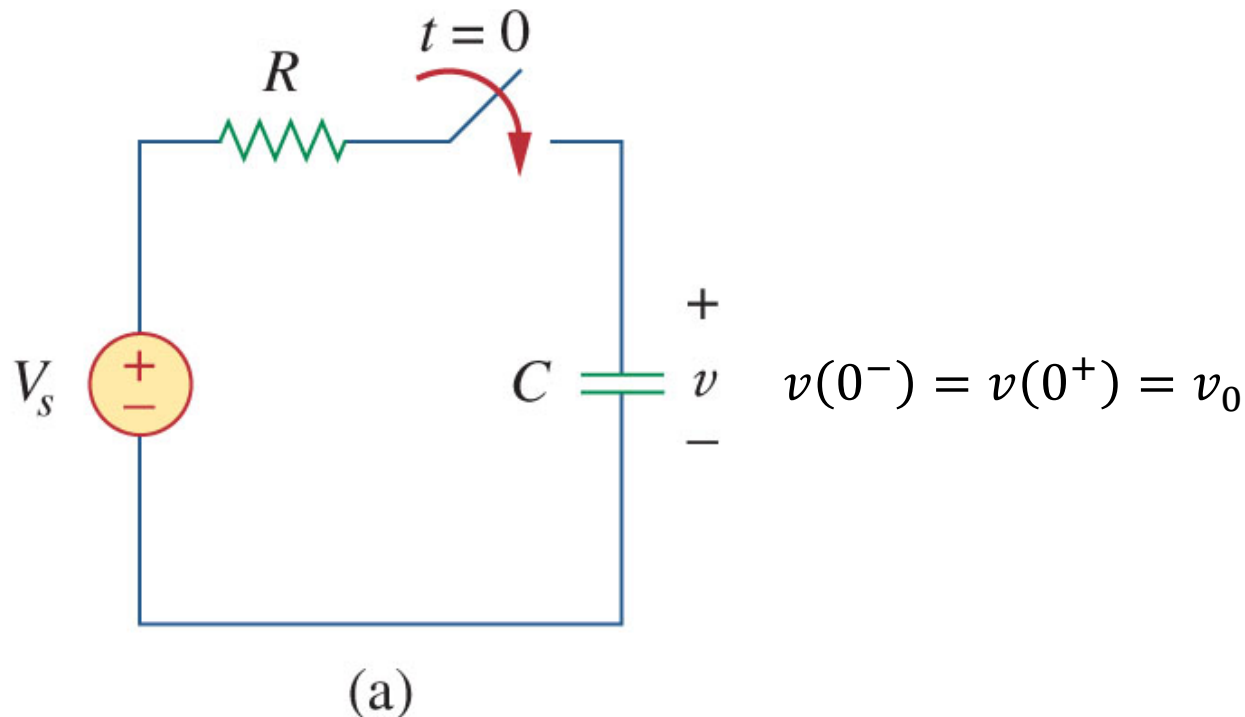
# Step Response of RC Circuit

- When a DC source is suddenly applied to a RC circuit, the circuit response is known as the step response.


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




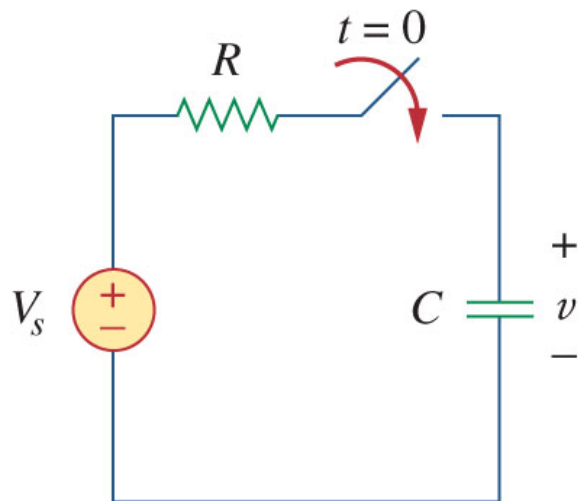
# Step Response of the RC Circuit

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




$$v(0^-) = v(0^+) = v_0$$


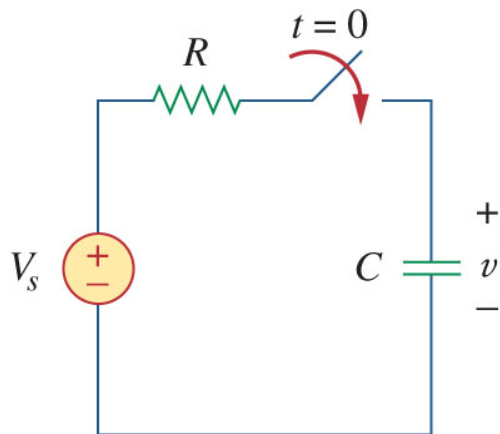
# Step Response of the RC Circuit


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$v(0^-) = v(0^+) = v_0$$

$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau} & t > 0 \end{cases}$$

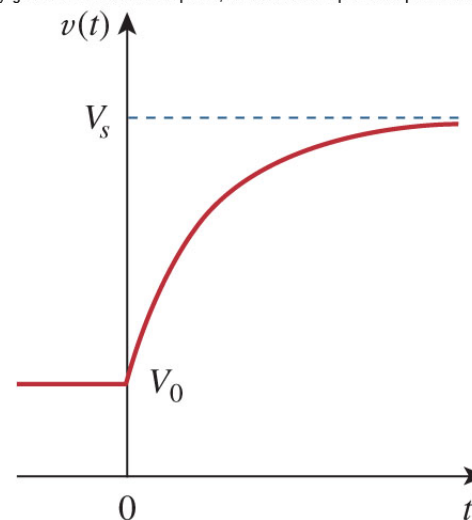Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




- This is known as the complete response, or total response.


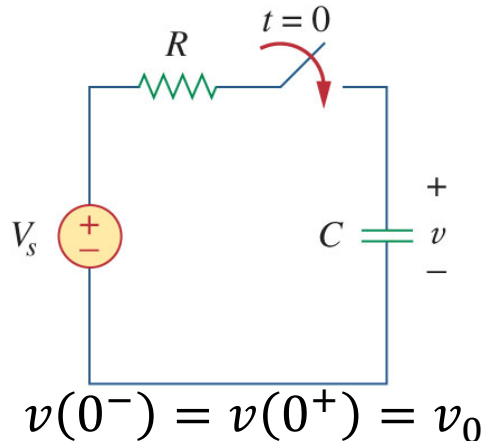
# Forced Response

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




- The complete response

$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau} & t > 0 \end{cases}$$

can be written as:

$$v = v_n + v_f$$

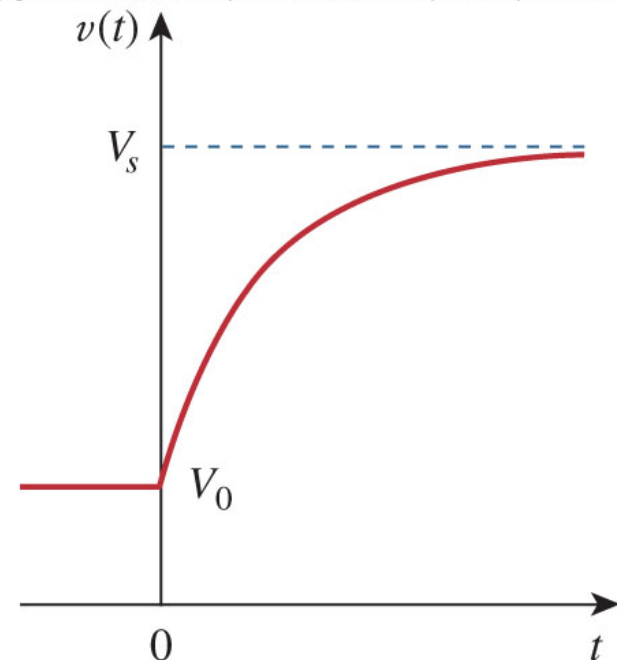
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




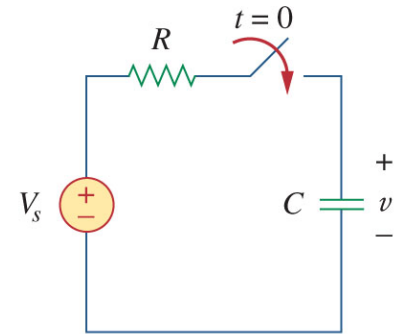
## Another Perspective

$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau} & t > 0 \end{cases}$$




- Another way to look at the response is to break it up into the transient response and the steady state response:

$$v(t) = \underbrace{v(\infty)}_{\text{steady } v_{ss}} + \underbrace{[v(0) - v(\infty)]e^{-t/\tau}}_{\text{transient } v_t}$$


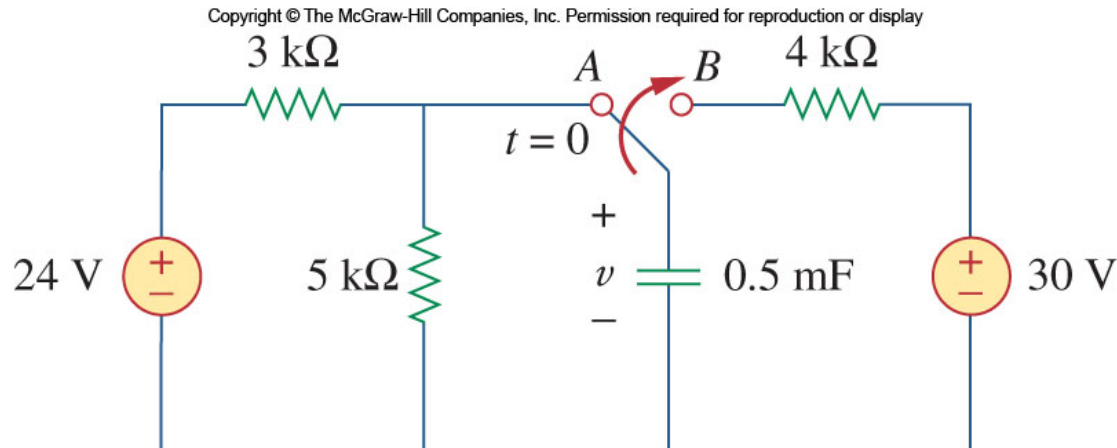
## Example


- The switch has been in position A for a long time. At  $t = 0$ , the switch moves to B. Find  $v(t)$ .




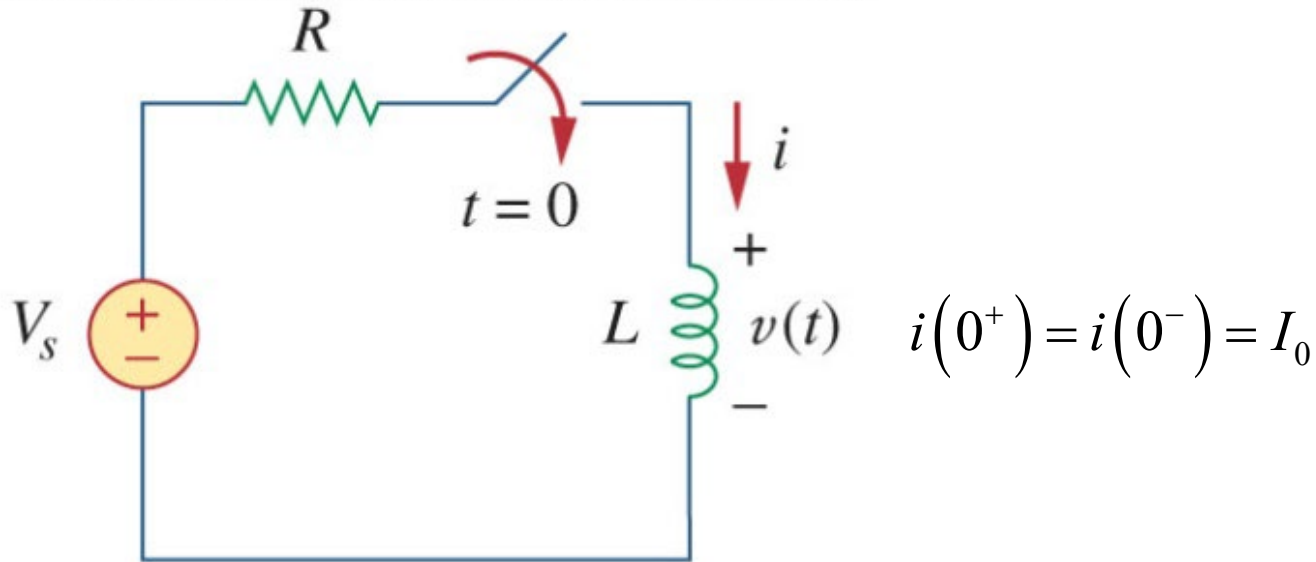
# Step Response of the RL Circuit

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



# Step Response of the RL Circuit



- We will use the transient and steady state response approach.
- We know that the transient response will be an exponential:

$$i_t = Ae^{-t/\tau}$$

- After a sufficiently long time, the current will reach the steady state:

$$i_{ss} = \frac{V_s}{R}$$

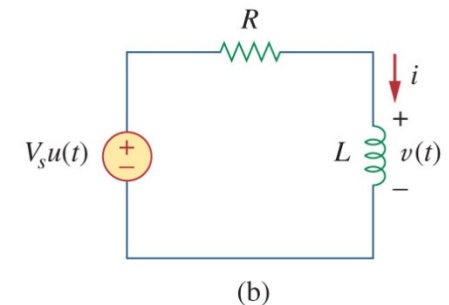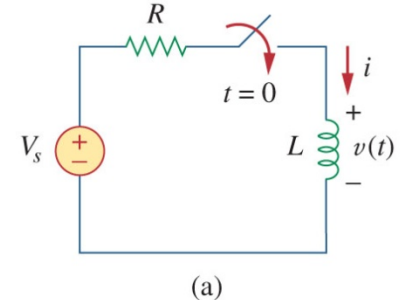
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display


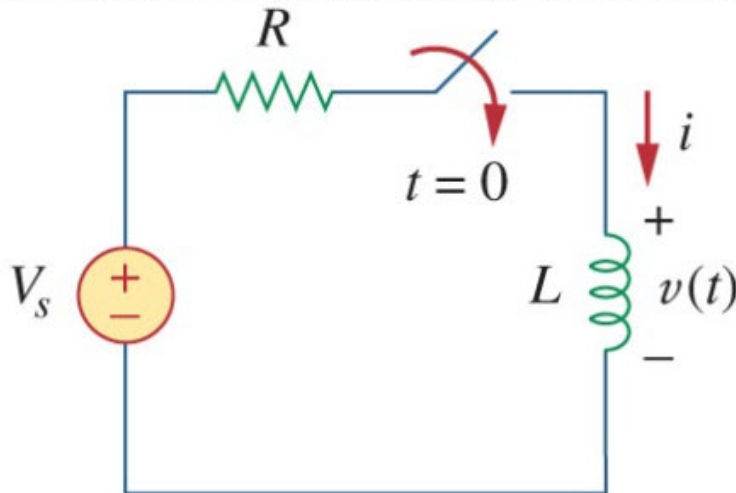
# Step Response of RL Circuit

- This yields an overall response of:

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$i = Ae^{-t/\tau} + \frac{V_s}{R}$$

$$i(0^+) = i(0^-) = I_0 \quad A = I_0 - \frac{V_s}{R}$$

$$i(t) = \frac{V_s}{R} + \left( I_0 - \frac{V_s}{R} \right) e^{-t/\tau}$$


# Response of a Circuit

- **Circuit (dynamic) response**


- the reaction of a certain voltage or current in the circuit to change, such as the adding of a new source, the elimination of a source, in the circuit configuration.

- **Transient response**

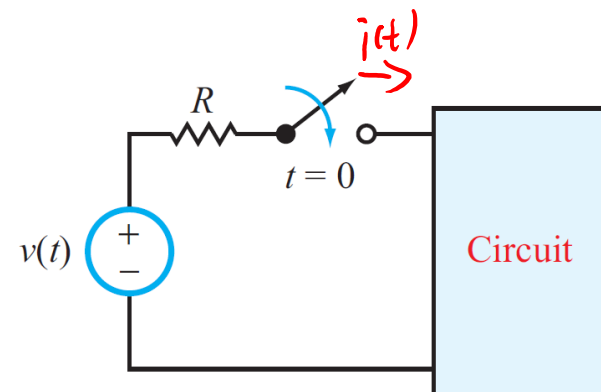- Behavior when voltage or current source are **suddenly** applied to or removed from the circuit due to switching.
- Temporary behavior



[Source: Berkeley]

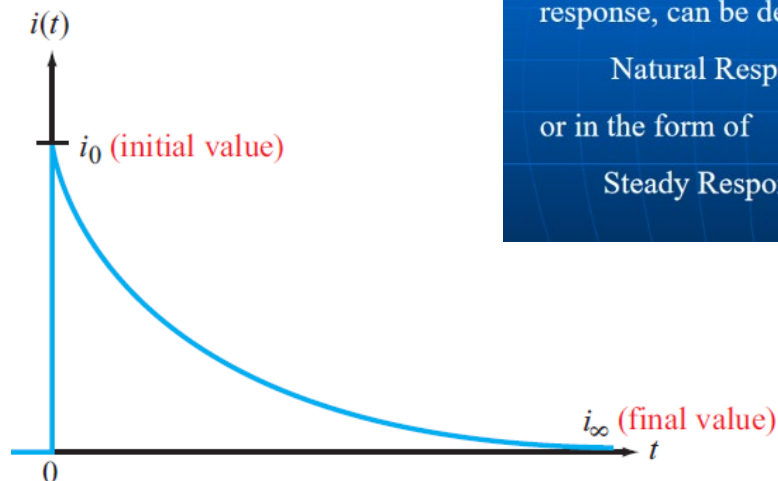

The solution of a linear circuit, called dynamic response, can be decomposed into

Natural Response + Forced Response

or in the form of


Steady Response + Transient Response


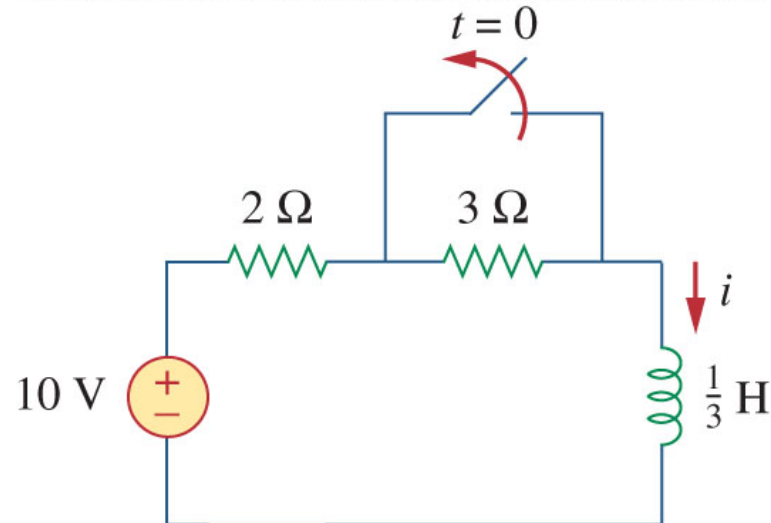
## Example

- Find  $i(t)$  in the circuit for  $t > 0$ . Assume that the switch has been closed for a long time.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





# General Procedure for Finding RC/RL Response

## 1. Identify the variable of interest

- For RL circuits, it is usually the inductor current  $i_L(t)$ .
- For RC circuits, it is usually the capacitor voltage  $v_c(t)$ .

## 2. Determine the initial value (at $t = t_0^-$ and $t_0^+$ ) of the variable

- Recall that  $i_L(t)$  and  $v_c(t)$  are continuous variables:

$$i_L(t_0^+) = i_L(t_0^-) \quad \text{and} \quad v_c(t_0^+) = v_c(t_0^-)$$

- Assuming that the circuit reached steady state before  $t_0$ : use the fact that **an inductor behaves like a short circuit in steady state** or that **a capacitor behaves like an open circuit in steady state**.





## Procedure (cont'd)

### 3. Calculate the final value of the variable (as $t \rightarrow \infty$ )


- Again, make use of the fact that **an inductor behaves like a short circuit in steady state ( $t \rightarrow \infty$ )** or that **a capacitor behaves like an open circuit in steady state ( $t \rightarrow \infty$ )**.
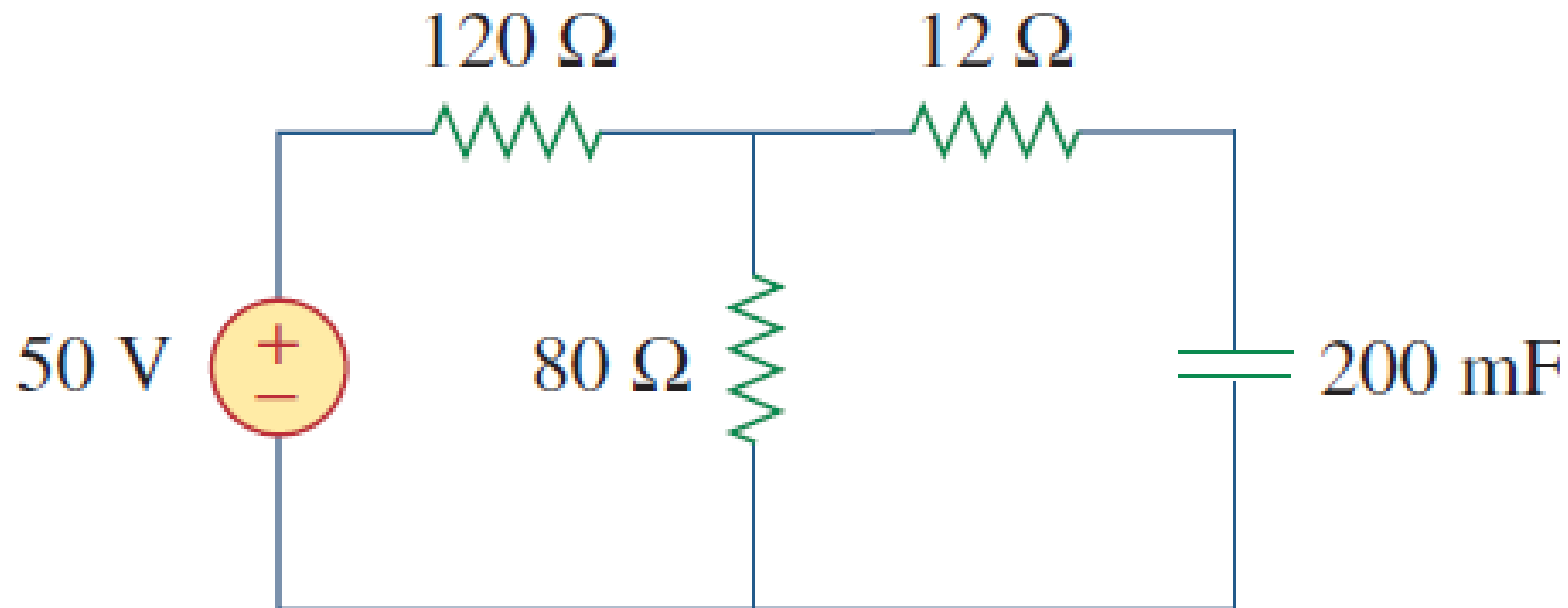
### 4. Calculate the time constant for the circuit

- **$\tau = CR$  for an RC circuit** where  **$R$**  is the Thévenin equivalent resistance “seen” by the capacitor.
- **$\tau = L/R$  for an RL circuit**, where  **$R$**  is the Thévenin equivalent resistance “seen” by the inductor.




Find the time constant for the  $RC$  circuit




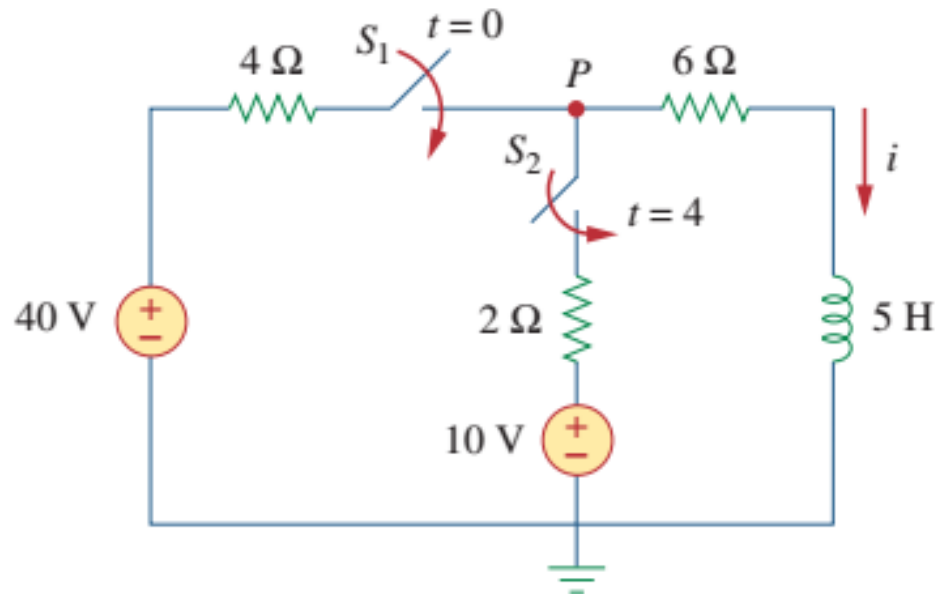
# Sequential switch

At  $t = 0$ , switch 1 in Fig. 7.53 is closed, and switch 2 is closed 4 s later. Find  $i(t)$  for  $t > 0$ . Calculate  $i$  for  $t = 2$  s and  $t = 5$  s.




We need to consider the three time intervals  $t \leq 0$ ,  $0 \leq t \leq 4$ , and  $t \geq 4$  separately. For  $t < 0$ , switches  $S_1$  and  $S_2$  are open so that  $i = 0$ . Since the inductor current cannot change instantly,


$$i(0^-) = i(0) = i(0^+) = 0$$



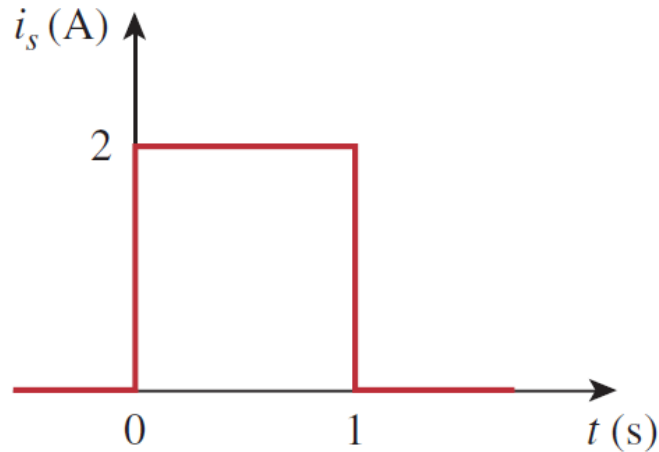**7.49** If the waveform in Fig. 7.116(a) is applied to the circuit of Fig. 7.116(b), find  $v(t)$ . Assume  $v(0) = 0$ .




(a)

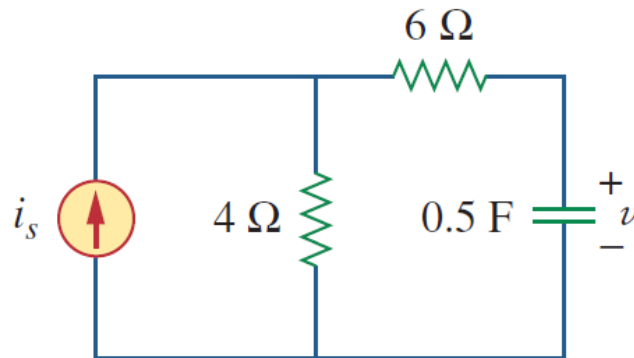

(b)

# 1<sup>st</sup> Order Circuit with OPA

**7.73** For the op amp circuit of Fig. 7.138, let  $R_1 = 10 \text{ k}\Omega$ ,  $R_f = 20 \text{ k}\Omega$ ,  $C = 20 \mu\text{F}$ , and  $v(0) = 1 \text{ V}$ . Find  $v_o$ .

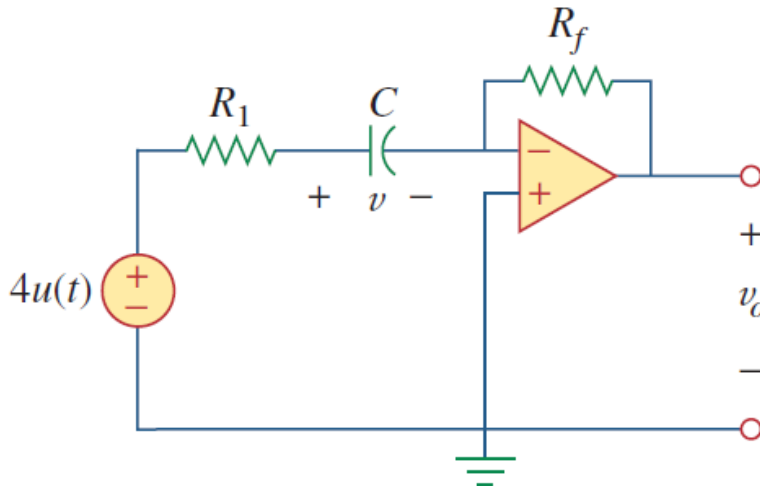


**Figure 7.138**

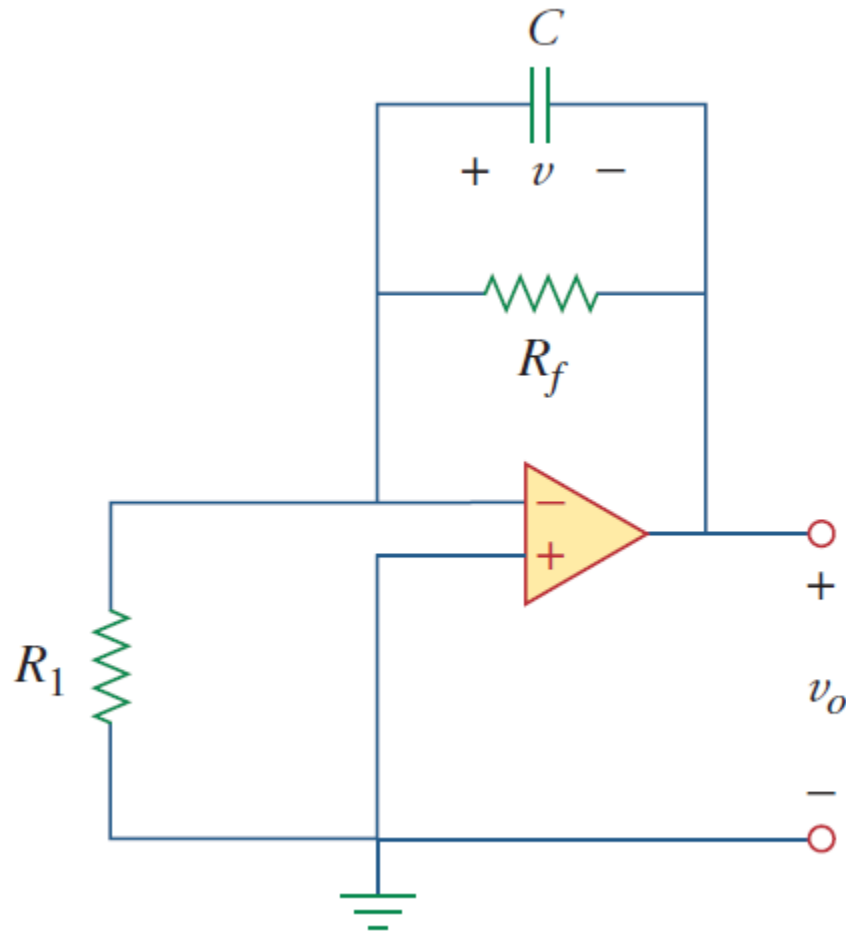For Prob. 7.73.




For the op amp circuit in Fig. 7.56, find  $v_o$  for  $t > 0$  if  $v(0) = 4$  V. Assume that  $R_f = 50$  k $\Omega$ ,  $R_1 = 10$  k $\Omega$ , and  $C = 10$   $\mu$ F.




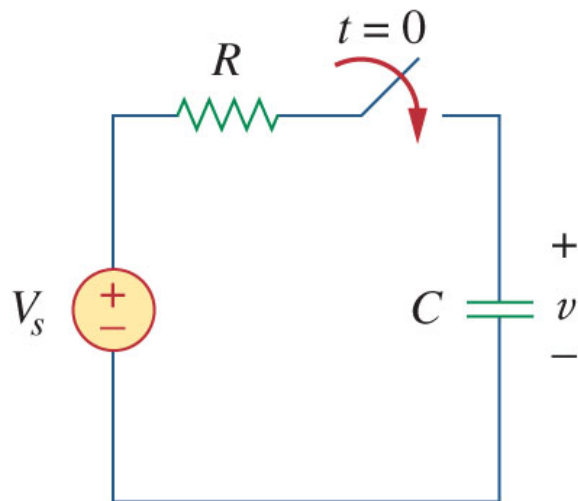
# Other kinds of excitations

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





$$V_s = e^{\omega t}, \quad \omega t, \quad V_s = \cos(\omega t)$$

$$v(0^-) = v(0^+) = v_0$$
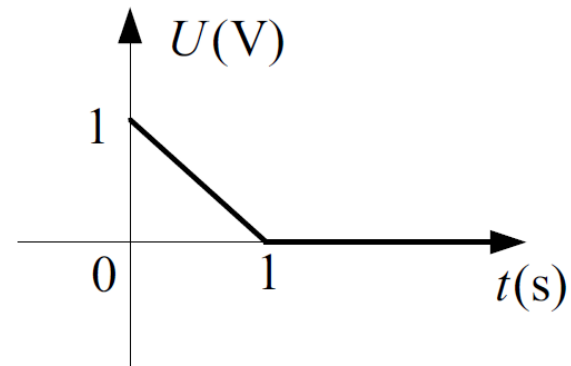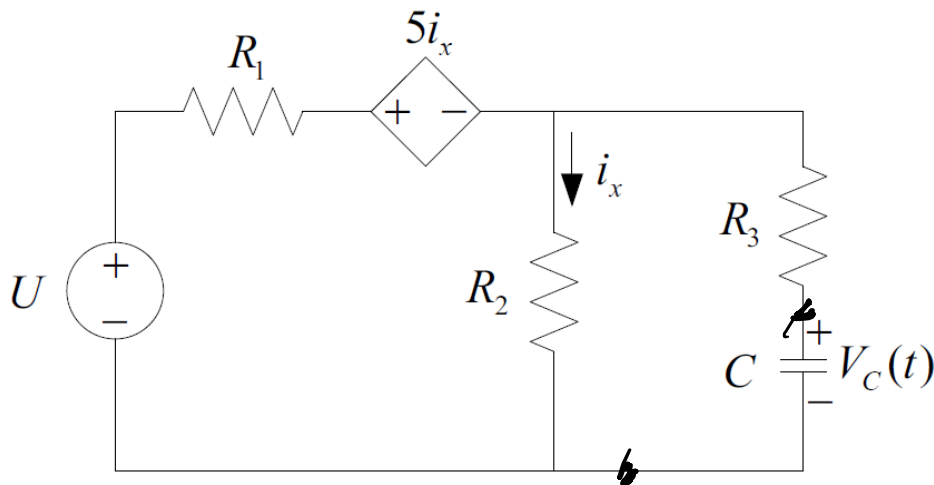
## Other kinds of excitations


In the circuit below,  $R_1 = 10\ \Omega$ ,  $R_2 = 5\ \Omega$ ,  $R_3 = 10\ \Omega$ ,  $C = 10\ \text{mF}$ . When  $t < 0$ , the input voltage ( $U$ ) is  $1\ \text{V}$ . When  $t = 0$ , the input voltage begins to change as shown in the plot below. When  $t > 1\ \text{s}$ ,  $U = 0$ . Assume that the circuit reaches steady state before  $t = 0$ . Determine the expression for  $V_C(t)$  when  $t \geq 0$ .







# Applications

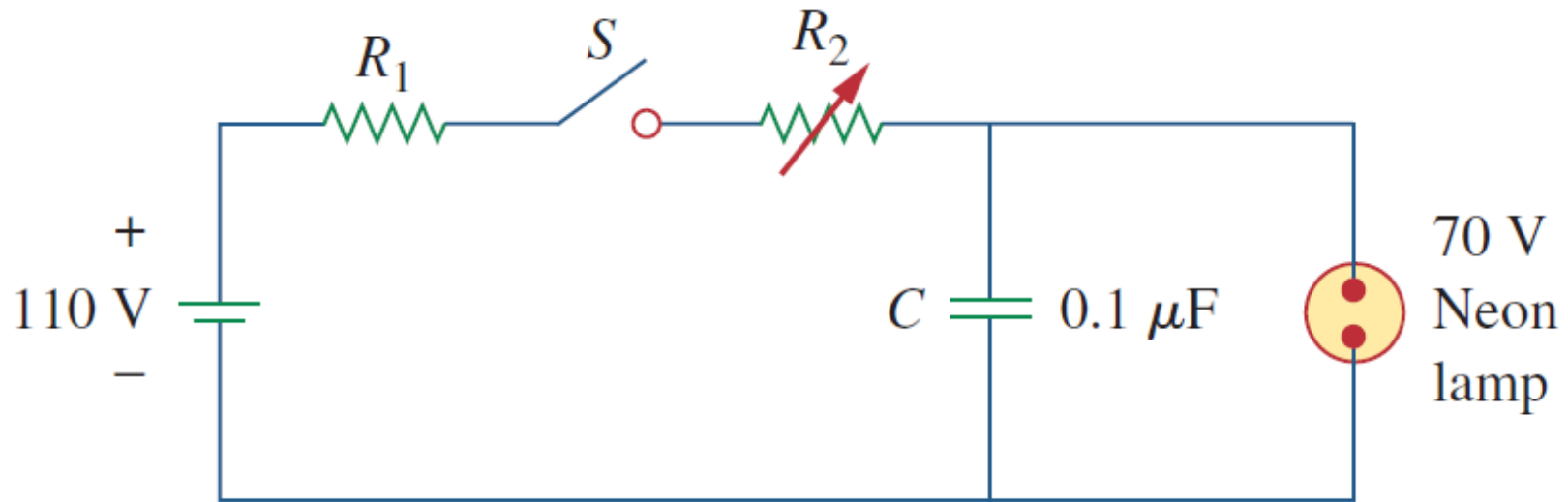



Activation of a switch at the time  $t = 0$  in a certain circuit caused the voltage across a  $L = 20 \text{ mH}$  inductor to exhibit the voltage response:

$$v(t) = 4e^{-0.2t} \text{ mV} \quad t > 0$$

Determine  $i(t)$  for  $t > 0$ , given the energy stored in the inductor at  $t = \infty$  is  $0.64 \text{ mJ}$ .

