

Homework 2

Due date: Mar. 14th

Turn in your homework in class

Rules:

- Please work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism!
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

1

[14 points] The circuit are shown in **Fig.1.a** and **Fig.1.b**.

- (a). Find the equivalent resistance R_{ab} between node a and node b in the circuit shown in **Fig.1.a**.
 (b). Find the power extracted from the current controlled current source in the circuit shown in **Fig.1.b**.

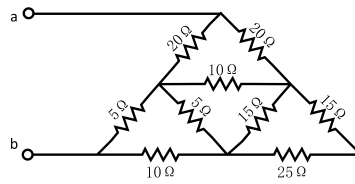


Figure 1: a

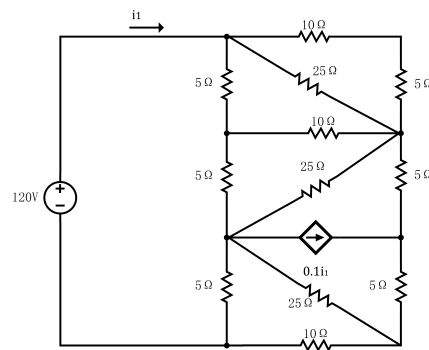


Figure 1: b

2

[15 points] The circuit is shown in **Fig. 2**.

- (a). Use superposition theorem to find V_0 .
- (b). Find the Thevenin equivalent circuit of the part framed by the dotted line, with terminals a and b .
- (c). Find the power absorbed by the voltage controlled current source.

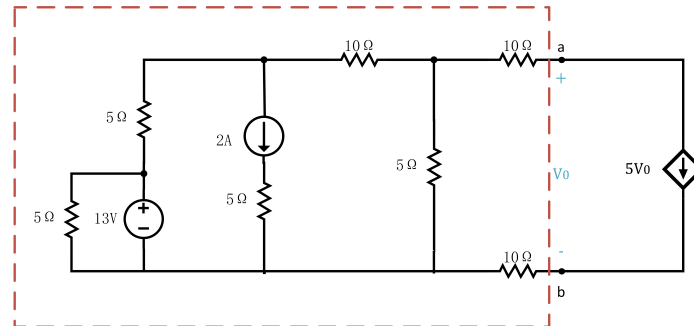


Figure 2:

3

[14 points] The circuit is shown in **Fig. 3**. Find the Thevenin and Norton equivalent circuit at terminals a and b .

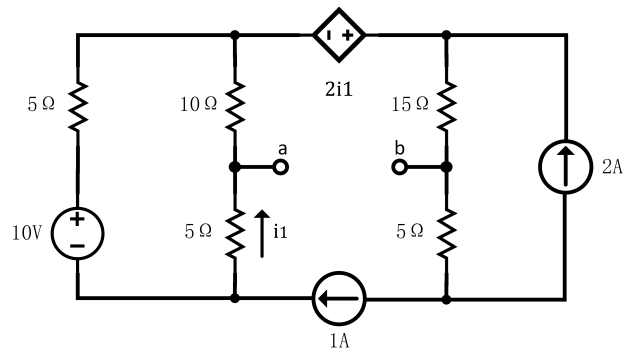


Figure 3:

4

[14 points] The circuit is shown in **Fig.4**. With varying resistant R , find the maximal power delivered to the resistant R . (Hint: you can use the Thevenin's theorem.)

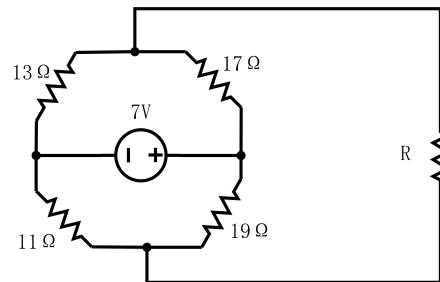


Figure 4:

5

[14 points] The circuit is shown in **Fig. 5**. $V_{cc} = 6V$. Assume the Op Amps are ideal, and OA_1 operates in its linear region.

- (a). Find the expression of v_{O1} in terms of R_1, R_2, R_3, R_4, V_1 . When $\frac{R_3}{R_1} = \frac{R_4}{R_2}$, determine the value of v_{O1} .
- (b). Assume $v_2 = v_3 = 2V$, $\frac{R_8}{R_5} = \frac{R_7}{R_6} = 2$. Find the value v_{O2} .

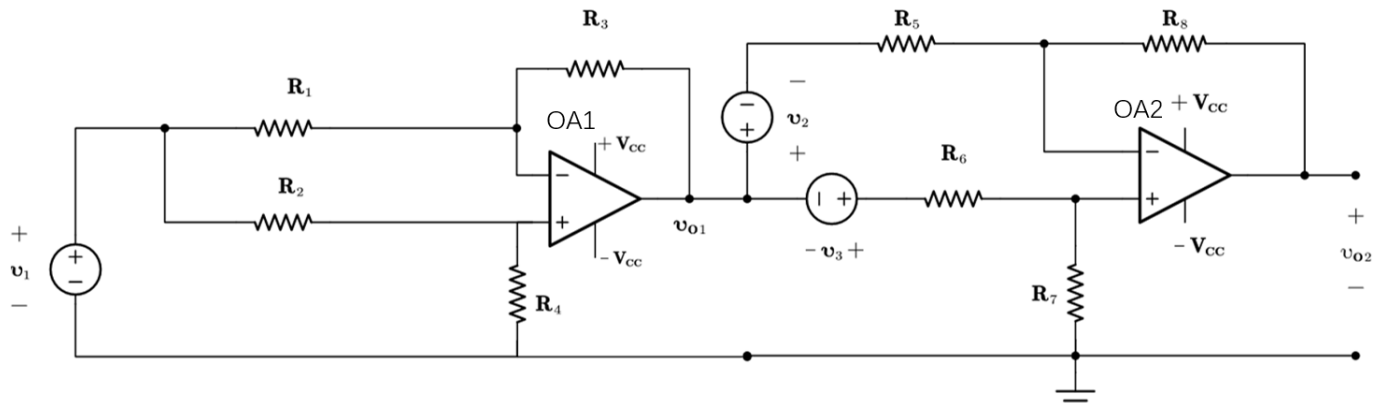


Figure 5:

6

[14 points] The circuit is shown in **Fig. 6**. The constitution of the operation amplifier is the circuit in blue (one can observe that the OA is not ideal). $A_{vo} = 100$ and $R_i = R_S$, $R_L = R_O$. $+V_{cc} = 10V$ and $-V_{cc} = -10V$ are the positive and negative power supply of the op amp.

- (a). Find the v_o for $v_s = 0.3V$
 (b). Find the v_o for $v_s = 0.5V$

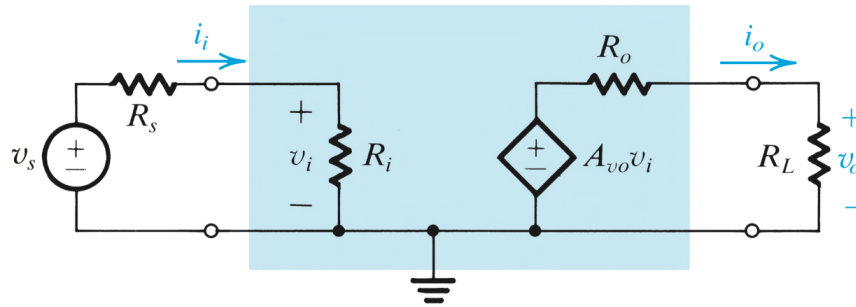


Figure 6:

7

[15 points] The circuit is shown in **Fig.7**. The operational amplifier is ideal and operates in its linear region. Find the output voltage v_o . (Hint: You can first find the Thevenin equivalent circuit of the part framed by the dotted line, with terminals a and b .)

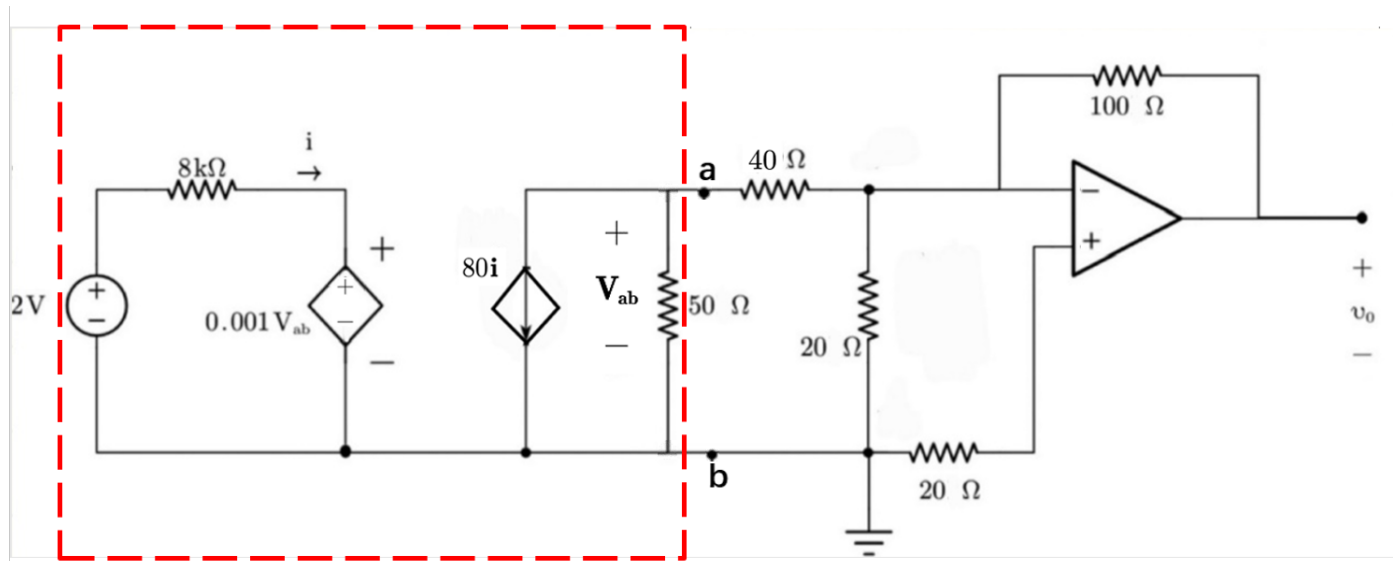


Figure 7: