


**Homework 1**

Due date: Feb. 28<sup>th</sup>, 2022, Monday  
Turn in your homework in class

Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

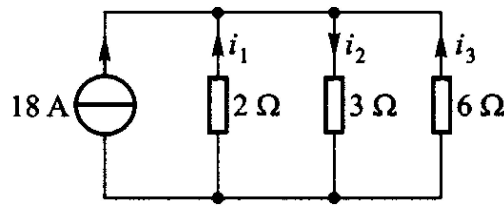1. Find the value of  $i_1$ ,  $i_2$ ,  $i_3$ .



6'

Using the shunt formula with resistors in parallel, we can get:


$$i_1 = \frac{-\frac{1}{2\Omega}}{\frac{1}{2\Omega} + \frac{1}{3\Omega} + \frac{1}{6\Omega}} \times 18A = -9A \quad 2'$$

$$i_2 = \frac{\frac{1}{3\Omega}}{\frac{1}{2\Omega} + \frac{1}{3\Omega} + \frac{1}{6\Omega}} \times 18A = 6A \quad 2'$$

$$i_3 = \frac{-\frac{1}{6\Omega}}{\frac{1}{2\Omega} + \frac{1}{3\Omega} + \frac{1}{6\Omega}} \times 18A = -3A \quad 2'$$

Note the relationship between the desired current and the direction of the reference current.

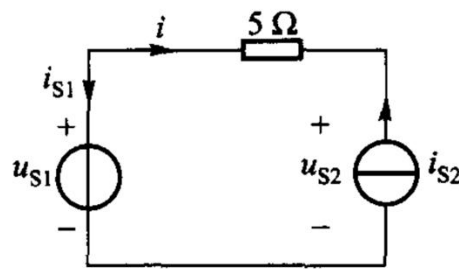2. Known that the voltage source is  $u_{s1} = 10V$ , and the current source is  $i_{s2} = 3A$ , find the power extracted from the voltage source and the current source.



$$\therefore i_{s1} = i_{s2} = 3A \quad 2'$$

The power extracted from the voltage source is:


$$P_{S1} = -u_{s1} \times i_{s1} = -10V \times 3A = -30W \quad 2'$$

$$\therefore u_{s2} = u_{s1} + 5\Omega \times i_{s2} = 10V + 5\Omega \times 3A = 25V \quad 2'$$

The power extracted from the current source is:

$$P_{S2} = u_{s2} \times i_{s2} = 25 \times 3A = 75W \quad 2'$$

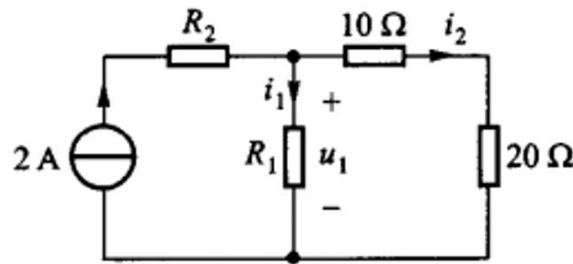3. Known that  $u_1 = 30V$ , find the value of the resistor  $R_1$ .



8'

The equation of KVL is:

$$u_1 = 10\Omega \times i_2 + 20\Omega \times i_2 = 30V \quad 2'$$

$$\Rightarrow i_2 = \frac{30V}{10\Omega + 20\Omega} = 1A \quad 2'$$


Using KCL equation we can deduce:

$$i_1 = 2A - i_2 = 1A \quad 2'$$

$$\text{So } R_1 = \frac{u_1}{i_1} = \frac{30V}{1A} = 30\Omega \quad 2'$$

The value of  $R_2$  does not affect the calculation result.

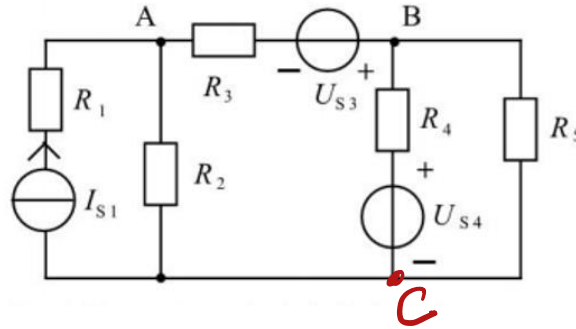4. Known that  $U_{S3} = U_{S4} = 10V$ ,  $I_{S1} = 10A$ ,  $R_1 = R_2 = 5\Omega$ ,  $R_3 = 4\Omega$ ,  $R_4 = R_5 = 2\Omega$ . Using nodal analysis, find  $U_{AB}$ .



12'


suppose point C is the potential reference point.

$$\begin{cases} (\frac{1}{R_2} + \frac{1}{R_3})V_A - \frac{1}{R_3}V_B = I_{S1} - \frac{U_{S3}}{R_3} & 4' \\ -\frac{1}{R_3}V_A + (\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5})V_B = \frac{U_{S3}}{R_3} + \frac{U_{S4}}{R_4} & 4' \end{cases}$$

$$\Rightarrow \begin{cases} V_A = 22.5V \\ V_B = 10.5V \end{cases} \quad 4'$$

$$U_{AB} = V_A - V_B = 12V$$

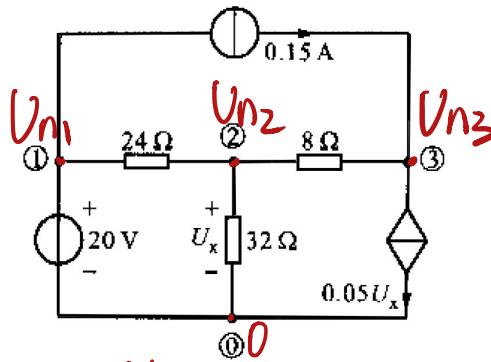5. Using nodal analysis, find the value of  $U_x$ .




The node voltage equations:

$$\begin{cases} V_{n2} = 20 & 2' \\ -\frac{1}{24}V_{n1} + \left(\frac{1}{24} + \frac{1}{32} + \frac{1}{8}\right)V_{n2} - \frac{1}{8}V_{n3} = 0 & 4' \\ -\frac{1}{8}V_{n2} + \frac{1}{8}V_{n3} = 0.15 - 0.05U_x & 4' \\ U_x = V_{n2} & 2' \end{cases}$$

$$\Rightarrow \begin{cases} 19V_{n2} - 12V_{n3} = 80 \\ -3V_{n2} + 5V_{n3} = 6 \end{cases}$$

$$\Rightarrow \text{So } U_x = V_{n2} = 8V \quad 2'$$

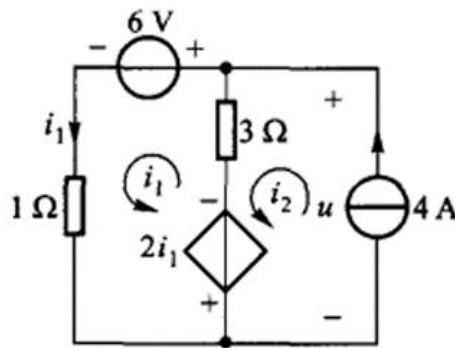6. Using mesh analysis, find the voltage  $u$  and the current  $i_1$ .




The mesh equation is:

$$\begin{cases} (1\Omega + 3\Omega) \times i_1 - (3\Omega) \times i_2 = -6V - (2\Omega) \times i_1 & 4' \\ i_2 = 4A & 4' \end{cases}$$

$$\Rightarrow (6\Omega) \times i_1 = -6V + 12V$$

$$\Rightarrow i_1 = 1A \quad 2' \quad u = 6V + 1\Omega \times 1A = 7V \quad 2'$$

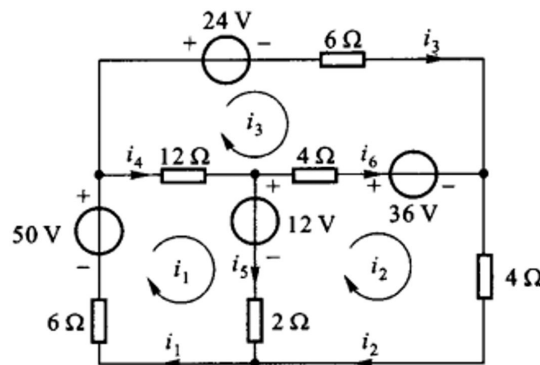7. Using mesh analysis, find  $i_1$ ,  $i_2$ ,  $i_3$ ,  $i_4$ ,  $i_5$ ,  $i_6$ .



The mesh equation is:

$$\begin{cases} (12\Omega + 2\Omega + 6\Omega)i_1 - (2\Omega)i_2 - (12\Omega)i_3 = -12V + 50V & 4' \\ -(2\Omega)i_1 + (4\Omega + 4\Omega + 2\Omega)i_2 - (4\Omega)i_3 = -36V + 12V & 4' \\ -(12\Omega)i_1 - (4\Omega)i_2 + (6\Omega + 4\Omega + 12\Omega)i_3 = -24V + 36V & 4' \end{cases}$$

$$\Rightarrow \begin{cases} 20i_1 - 2i_2 - 12i_3 = 38 \\ -2i_1 + 10i_2 - 4i_3 = -24 \\ -12i_1 - 4i_2 + 22i_3 = 12 \end{cases}$$

$$\Rightarrow i_1 = 3A \quad i_2 = -1A \quad i_3 = 2A$$

using KCL:  $i_4 = i_1 - i_3 = 1A$

$$i_5 = i_1 - i_2 = 4A$$


$$i_6 = i_2 - i_3 = -3A$$

we can use KVL equation of the outer mesh to check the result.

$$(6\Omega) \times 3A - 50V + 24V + (6\Omega) \times 2A + (4\Omega) \times (-1A) = 0$$



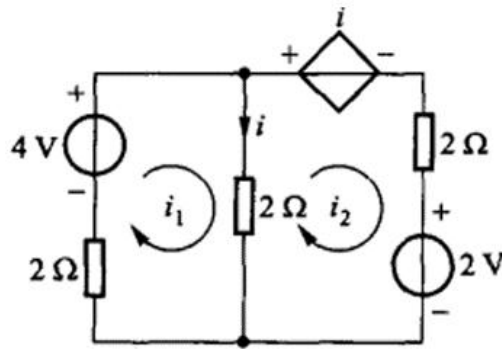8. Using mesh analysis, find  $i_1$ ,  $i_2$ .



The mesh equation is:

$$(2\Omega + 2\Omega) \times i_1 - (2\Omega) \times i_2 = 4V$$

$$-(2\Omega) \times i_1 + (2\Omega + 2\Omega) \times i_2 = -2V - (1\Omega) \times i$$

Supplementary equation:  $i = i_1 - i_2$

$$\Rightarrow \begin{cases} 4i_1 - 2i_2 = 4A \\ -i_1 + 3i_2 = -2A \end{cases} \Rightarrow i_1 = 0.8A \quad i_2 = -0.4A$$